SM - 420

II Semester B.Sc. Examination, May/June 2018	
(CBCS) (Fresh + Repeaters) and the addition of the	
(2014-15 and Onwards) and energy (a	
ELECTRONICS – II	
Electronics Circuits and Special Purpose Devices	
Time : 3 Hours crossover distortion ? How it	Max. Marks : 70
Instructions : Answer all the or questions from I Part – C .	uestions from Part – A , any five Part – B and any four questions from
Note : It is required to answer all the questions of Part – A in any one page answering the same questions multiple times will not be considered for evaluation.	
6 a) Mentelstdivitiwe sideteonow PART	- A deacloopsidivitational destate
1. Answer all the subdivisions : BRAKED	(15×1=15) ristable multivibrator
i) An amplifier has a power gain of 100	. Its gain in dB is
a) 10 dB b) 20 dB	c) 30 dB d) 40 dB
 ii) In an RC coupled amplifier, the voltage gain over mid-frequency range a) Changes abruptly with frequency b) Is constant c) Changes uniformly with frequency d) None of the above 	
iii) A JFET is a driven device	2+Siii) To turn on UJT, the forward bias e
a) Current	b) Voltage Distov thiog keep entry
c) Power	d) Both current and voltage
iv) In a Class B power amplifier, the maximum efficiency is	
a) 25% b) 78.5%	c) 50.5% d) 100%
v) The size of a power transistor is made considerably large to	
a) Provide easy handling	b) Dissipate heat
c) Facilitate connections	d) Make easy to use
vi) A tuned amplifier is ampl	ifier. Solar cell ifier.
a) Narrowband	b) Wideband
c) Direct coupled	d) Impedance coupled
 vii) Differential gain means a) Amplifying the difference between b) Amplifying the sum of inputs c) Attenuating the difference between 	Answer any five questions :
d) Attenuating the sum of inputs	b) Classify the amplifier based on dif

SM - 420

- viii) The tail current equals the sould a deered (20 a) Difference between the two emitter currents b) Sum of the two emitter currents c) Collector current divided by current gain d) Collector voltage divided by collector resistance ix) Negative feedback in an amplifier a) Reduces the voltage gain b) Reduces the distortion c) Both a) and b) and b a base of the descent of the collage gain x) The Hartley oscillator uses b) Two inductors a) One inductor d) Four inductors c) Three inductors xi) A multivibrator which consist of two quasi stable state is called b) Monostable multivibrator a) Bistable multivibrator c) Tristable multivibrator d) Astable multivibrator xii) A MOSFET can be operated with a) Negative gate voltage only b) Positive gate voltage only a second and here below of the second c) Positive as well as negative gate voltage d) Zero voltage only to enable to vone post driv viewolinu second to to xiii) To turn on UJT, the forward bias on the emitter diode should be _____ the peak point voltage. b) Equal to a) Less than d) None of the above c) More than xiv) A TRIAC is equivalent to two SCRs in b) Series a) Parallel
 - d) Series parallel a) Provide easy
 - xv) For satellites the source of energy is
 - a) Solar cell
 - c) Edison cells
- b) Fuel cells

(5×7=35)

- d) Cryogenic storage
- belguos esasbegal PART B

Answer any five questions :

c) Inverse parallel

- 2. a) With an equivalent circuit, derive an expression for voltage gain of a CE amplifier. Also write an expression for Z_{in} and Z_{out}.
 - b) Classify the amplifier based on different types of coupling. (b (6+1)

SM - 420

- 3. a) With a circuit diagram, explain the working of a common source JFET Given, g, = 4mS and r, = 10 kQ. Also find the voltage gain, if 29 and r b) Draw the circuit diagram of a Darlington amplifier and mention its characteristic features. (4+3)4. a) What is crossover distortion ? How it can be minimized ? b) Explain the frequency response curve of a double tuned amplifier for (3+4) critical and tight coupling. 5. a) Derive an expression for Q-point of a dual input balanced output differential amplifier. b) What is a current mirror ? Mention its effect on differential gain. (5+2)6. a) Mention the advantages of a negative feedback configuration over a positive feedback configuration. b) Derive an expression for the voltage gain of a voltage series negative (2+5)feedback amplifier. 7. a) What are damped and undamped oscillations ? b) Draw the equivalent circuit of a piezo electric crystal. With a circuit diagram, explain the working of a crystal oscillator. 8. With a circuit diagram, explain the working of a SCR full wave rectifier and derive an expression for its average load voltage and current. 9. a) Write the symbol of TRIAC and DIAC. Mention its applications. b) Draw the V-I characteristics curves of varactor diode and photo diode. (3+4) PART – C $(4 \times 5 = 20)$ Answer any four questions : 10. A three stage RC coupled amplifier produces an output voltage of 100V for the input voltage of 5 mV. The voltage gain of the first stage is 100 and the output voltage of the second stage is 20V. Calculate the : i) output voltage of first stage ii) voltage gain of second and third stage
 - iii) express the overall voltage gain in dB.

11. Calculate the voltage gain of Common Source JFET amplifier shown in figure. Given, $g_m = 4mS$ and $r_d = 10 k\Omega$. Also, find the voltage gain, if 20 k Ω load resistance is connected across the output terminals.



- 12. In a dual input balanced output differential amplifier, $I_E = 2mA$, $R_C = 1.8k\Omega$, $R_E = 470\Omega$ and $\beta = 150$. Calculate :

 - iii) Input impedance
- iv) CMRR.
- 13. In a transistor Colpitt's oscillator, $C_1 = C_2 = 0.1 \ \mu\text{F}$ and the inductance used in the tank circuit is 500 μ H. Calculate the frequency of oscillations. If the value of inductance is doubled, calculate the frequency of oscillations.
- 14. The UJT has $\eta = 0.65$ and $R_{_{BB}} = 8k\Omega$. Calculate :
 - i) R_{B1} and R_{B2} isoliggs at notine M.OAIG bia OAIGT to lodmy entremain (a, b)
- (Appli) Peak point voltage (V_P).
 - If R_{BB} is changed to $4k\Omega$, calculate the same.
 - Given $V_{BB} = 10V$ and $V_{D} = 0.7 V$. TRAS
- 15. Each of the SCRs used in a full wave rectifier will fire at 100V for a gate current of 1mA. If the peak a.c. voltage across each SCR is 200 V, calculate the :
 - input voltage of 5 mV. The voltage gain of the first stage is 10 algae gain (i.i.
 - ii) Average output voltage and etaluolaO .VOS all egate bnoose and to egation
 - iii) Average current for a load resistance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the sector will be defined by the distance of 220Ω and the distance of 220
 - iv) Power output. while an expression of the bird bas become to ning egation (ii)

(iii) express the overall voltage gain in dB